

Exercise Worksheet 2

25. Oktober 2011

Exercise 1

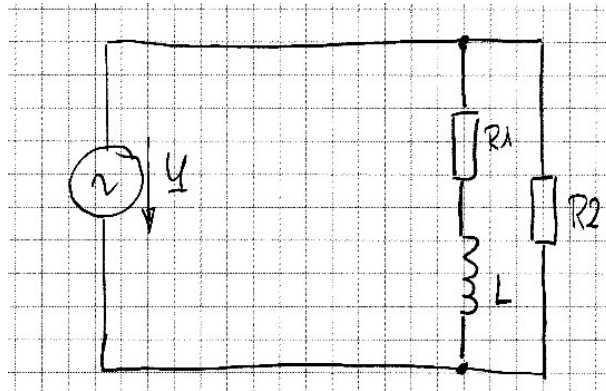


Abbildung 1: Complex Circuit

The values of the components and parameters are given:

- $R_1 = 20\Omega$
- $R_2 = 80\Omega$
- $L = 191mH$
- $f = 50Hz$
- $\underline{U} = 230V$

Part A

Please calculate the:

- Real Power
- Reactive Power
- Apparent Power

Part B

Please calculate the power factor

Part C

- calculate the component for power factor correction ($\cos \varphi = 1$)
- calculate the component for power factor correction ($\cos(\varphi) = 0.95$)

Exercise 2

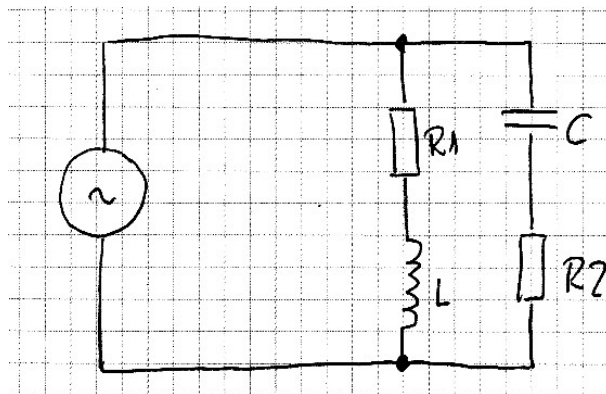


Abbildung 2: Complex Circuit

The values of the components and parameters are given:

- $R_1 = 40\Omega$
- $R_2 = 30\Omega$

- $L = 127.32mH$
- $C = 159.15\mu F$
- $f = 50Hz$
- $\underline{U} = 230V$

Part A

Please calculate the:

- Real Power
- Reactive Power
- Apparent Power

Part B

Please calculate the power factor

Part C

- calculate the component for power factor correction ($\cos(\varphi) = 1$)

Exercise 3

The name plate of a motor gives us following data

- Rated power $P = 0.8kW$
- Rated voltage $U = 380V$
- Rated frequency $f = 50Hz$
- $\cos(\varphi) = 0.78$

Please calculate the component for power factor correction ($\cos(\varphi) = 1$)